

(Following Paper ID and Numbers to be filled in your Answer books)

Paper ID:

--	--	--	--	--	--

Roll No:

--	--	--	--	--	--	--	--	--	--

B.Tech

EXAMINATION, 2015-16

Subject: Integrated Circuits

Code: NEC 501

[Time: 3 Hours]

[Total Marks: 100]

SECTION-A



Q.1 Attempt all parts. All parts carry equal marks. Write answer of each part in short. (2 x 10=20)

- What are the device parameters for the IC-741?
- List out the properties of current mirror circuit.
- What do you mean by unity gain bandwidth?
- Name the IC number used for phase locked loop and comparators.
- Write down the applications of V-I and I-V converter.
- Write down the two resistive techniques for DAC and name the CMOS version of the 555 timer.
- Calculate the time period of astable multivibrator having $R_1 = R_2 = 2k\Omega$, $R = 4k\Omega$ and $C = 0.01\mu F$
- What is a Sallen-key filter?
- Define the term delay-power product for digital logic family.
- What are the applications of analog multiplier?

SECTION-B

Note: Attempt any 5 questions from this section. (10 x 5=50)

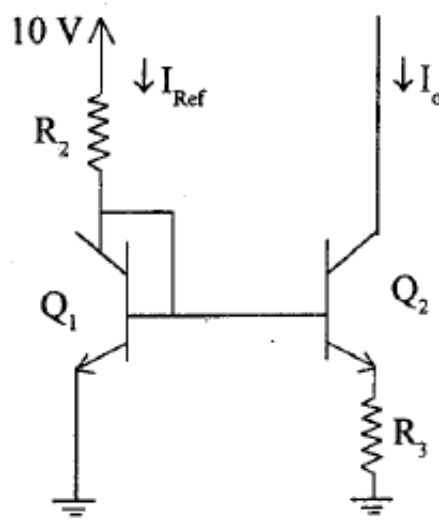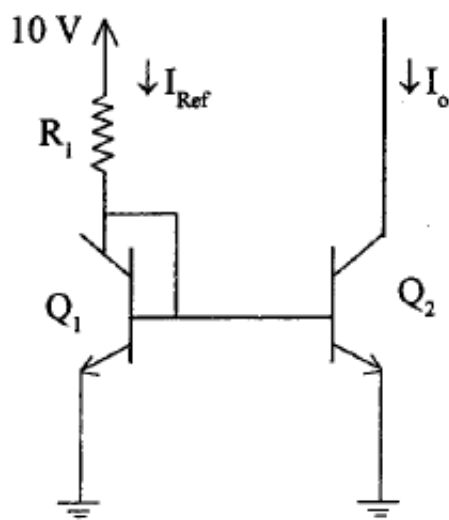- Q.2** With the help of a neat circuit diagram explain the operation of Widlar current source. Figure given below shows two circuit for generating a constant current $I_o = 10\mu A$ which operates from a 10V supply. Determine the values of the required resistor assuming the $V_{BE} = 0.7V$ at a current of 1mA and neglecting the effect of finite β .



- Q.3 Explain the generation of triangular waveform in detail.
- Q.4 Draw and explain the working of instrumentation amplifier. Find out input and output voltage relationship for instrumentation amplifier.
- Q.5 Draw and explain the circuit diagram and waveforms for one shot multivibrator using op-amp. Also derive the expression for its time period.
- Q.6 Write down the short notes on the R-2R ladder D/A converter.
- Q.7 Give truth table and CMOS realization (AOI and OAI both) of following gate: $F = \bar{A}B + A\bar{B}$.

- Q.8 Draw & explain the operation of antilog amplifier circuit. Find out the expression for its output voltage equation. Also discuss applications of log and antilog amplifiers.
- Q.9 Why ADC is required? Explain the working of Dual Slope ADC with the help of circuit diagram and obtain expressions for integrator output at distinct input signals.

SECTION-C

Note: Attempt any 2 questions from this section. (15 x 2=30)

- Q.10 Write down the short notes on the following:

- Functional block diagram of 555 timer
- Monolithic PLL

- Q.11 Design the high-pass filter at a cutoff frequency of 1kHz with a passband gain of 2. Also explain the DC analysis of input stage of IC 741 in detail.
- Q.12 Derive the expression for the noise margin of the CMOS inverter in term of V_{IH} , V_{IL} , V_{OL} and V_{OH} .